

Homework

- Reading: Chapter 8
- Exercises: Chapter 8, all
- Due Friday, 9/28

COS 140: Foundations of Computer Science

Adders

Fall 2018

Adders	3
What is an adder?	3
Why Study Adders?	4
How Do We Do Addition?	5
Binary Numbers	6
A Closer Look at Our Digital System	7
In a Binary System...	8
From decimal to binary	9
Algorithm	10
Adders	13
Adding in computer.	13
Truth Table	14
Circuit.	15
Insight.	16
Half-Adder	17
Full Adder	18
Multi-bit Adders	22
Multi-bit Adders	22
Ripple Carry	23
Carry Lookahead.	24
Trade-offs	27
Mixed Carries	28
Conclusion	29

What is an adder?

- An adder is a logic circuit that adds binary numbers
- Could add two 1-digit numbers or two n -bit numbers

Copyright © 2002–2018 UMaine Computer Science Department – 3 / 29

Why Study Adders?

- Interesting example of a [combinational circuit](#).
 - Circuit whose output relies solely on its inputs.
 - Perform an important function for the computer.
 - ▷ Addition is also basis for other arithmetic functions in the computer (subtraction, multiplication, etc.)
 - ▷ Would like the function done in hardware so it is done quickly.

Copyright © 2002–2018 UMaine Computer Science Department – 4 / 29

How Do We Do Addition?

1. Write down numbers that will be added using symbols from 0 to 9.
2. Use arithmetic facts to add numbers in a column. If more than 9, carry the most significant digit to the next column.

Copyright © 2002–2018 UMaine Computer Science Department – 5 / 29

Numbers and Digital Logic

- Symbols will correspond to the 0 or 1 that is the input or output of the circuit. So, have 2 symbols to work with, not 10.
- Create a **binary** system that is like our **digital** system.

Copyright © 2002–2018 UMaine Computer Science Department – 6 / 29

A Closer Look at Our Digital System

- Have 10 digits: 0–9
- Have “places” for 1’s, 10’s, 100’s, 1000’s, 10,000’s, etc. that correspond to powers of 10.
 - $10^0 = 1; 10^1 = 10; 10^2 = 100; 10^3 = 1000; 10^4 = 10,000$
- To find the value of a number, add all the digits times their place values.
 - $359 = 9 \times 1 + 5 \times 10 + 3 \times 100$

Copyright © 2002–2018 UMaine Computer Science Department – 7 / 29

In a Binary System...

- Have 2 digits: 0 and 1

- Places correspond to powers of 2:

2^0	1	2^4	16	2^8	256
2^1	2	2^5	32	2^9	512
2^2	4	2^6	64	2^{10}	1024
2^3	8	2^7	128	2^{11}	2048

- To find the value, add all the 1's and 0's times their place values.
 - Example from lecture: $10110 = ?$

Copyright © 2002–2018 UMaine Computer Science Department – 8 / 29

From decimal to binary

Given: n , a decimal number

1. First find the largest power of two less than n ; let i be the exponent
2. Write down a 1, and $n = n$ minus that power of two
3. Decrement i to work on next-lower binary digit; if $i = 0$, we're done
4. If $2^i > n$, then there should be a 0 for that power of two; write that down, and go to 3
5. Else, if $2^i = n$, then write 0s for all the rest of the digits, and you're done
6. Otherwise ($2^i < n$), write a 1, since this power of 2 "fits" in n ; $n = n - 2^i$, and go to 3

Copyright © 2002–2018 UMaine Computer Science Department – 9 / 29

The algorithm

```
1: Algorithm Convert( $d$ )
2:   Input:  $d$ , a decimal number
3:   Output: the binary version of  $d$ 
4:   Let  $n$  be largest whole number such that  $2^n \leq d$ 
5:   while  $n \geq 0$  do
6:     if  $d = 2^n$  then
7:       Output 1 followed by  $n - 1$  0s
8:       return
9:     else if  $d < 2^n$  then
10:      Output 0
11:       $n = n - 1$ 
12:     else
13:      Output 1
14:       $d = d - 2^n$ 
15:       $n = n - 1$ 
16:     end if
17:   end while
18: End.
```

Copyright © 2002–2018 UMaine Computer Science Department – 10 / 29

Example

359	$2^8 < d < 2^9, \therefore n = 8 \Rightarrow$	1
- 256	Subtract $2^8 = 256, n = 7$	
<hr/> 103	$2^7 > d; n = 6 \Rightarrow$	0
	$2^6 < d \Rightarrow$	1
- 64	Subtract $2^6 = 64, n = 5$	
<hr/> 39	$2^5 < d \Rightarrow$	1
- 32	Subtract $2^5 = 32, n = 4$	
<hr/> 7	$2^4 > d; n = 3 \Rightarrow$	0
	$2^3 > d; n = 2 \Rightarrow$	0
	$2^2 < d \Rightarrow$	1
- 4	Subtract $2^2 = 4, n = 1$	
<hr/> 3	$2^1 < d \Rightarrow$	1
- 2	Subtract $2^1 = 2, n = 0$	
<hr/> 1	$2^0 = d, \Rightarrow$	1

So $359_{10} = 101100111_2$

Copyright © 2002–2018 UMaine Computer Science Department – 11 / 29

There are only 10 kinds of people in this world. Those that understand binary and those that don't.
– graduate student's T-shirt

Copyright © 2002–2018 UMaine Computer Science Department – 12 / 29

Adders

13 / 29

Use Arithmetic Facts to Add Numbers

- Addition results from applying facts about arithmetic to numbers
- For the computer to use arithmetic facts, we need to construct a circuit.
- So: start with a truth table.
- Construct a truth table for all of the inputs, including the possible carry.

Copyright © 2002–2018 UMaine Computer Science Department – 13 / 29

Truth Table for Addition


Carry-in	A	B	Carry-out	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Copyright © 2002–2018 UMaine Computer Science Department – 14 / 29

Circuit from truth table


- Can we find a circuit for this? A minimal circuit?
- Karnaugh map for carry out:

C_in	A	B	C_out	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Karnaugh map for sum out:

C_in	A	B	C_out	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Copyright © 2002–2018 UMaine Computer Science Department – 15 / 29

A better idea


- So minimization using Karnaugh maps, algebraic substitution – not so good!
- Can we do better?
- Maybe – inspect the truth table
- Things are simplified when we look at just A and B as inputs:

A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- Sum and carry – both correspond to basic operations/gates
- Sum = $A \oplus B$
- Carry = AB

Copyright © 2002–2018 UMaine Computer Science Department – 16 / 29

Half-Adder

 

We can create a very simple circuit to add A and B.
[Half-adder](#) because only does half the job.

We need a *full adder* that adds $A + B + C_{in}$.

Copyright © 2002–2018 UMaine Computer Science Department – 17 / 29

Full Adder

- $A, B, C_{in} \rightarrow S$ (sum), C (carry out)
- Can we use a half-adder + additional logic get outputs?
- Half adder: $A, B \rightarrow S_h, C_h$
- Generating S (sum):
 - $S = A + B + C_{in} = (A + B) + C_{in} = S_h + C_{in}$
 - Use another half-adder: $S_h, C_{in} \rightarrow S_{h2} = S$

Copyright © 2002–2018 UMaine Computer Science Department – 18 / 29


Full Adder

- When is C (carry out) = 1? When $A + B + C_{in} \geq 10_2$
 - Case 1: $A + B = 10_2$
 - ▷ Doesn't matter what C_{in} is: $C = 1$
 - ▷ In this case: $C_h = 1$
 - Case 2: $A + B = 1$ and $C_{in} = 1$
 - ▷ This means that $S_h = 1, C_{in} = 1$
 - ▷ In this case, carry out of second half-adder $C_{h2} = 1$
- So $C = 1$ when either either or both half-adder carries is 1
- $\therefore C = C_h \vee C_{h2}$

Copyright © 2002–2018 UMaine Computer Science Department – 19 / 29


Full Adder

 We can create a full adder by putting two half adders together as described above.



Copyright © 2002–2018 UMaine Computer Science Department – 20 / 29

Full Adder

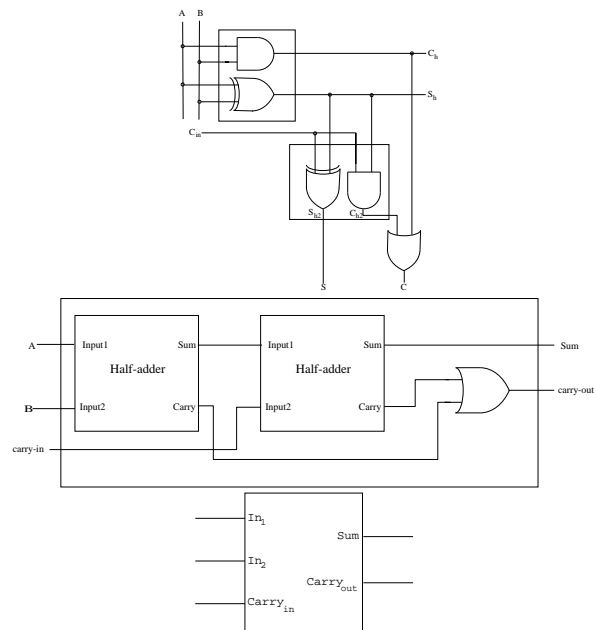

Copyright © 2002–2018 UMaine Computer Science Department – 21 / 29


Creating Multi-Bit Adders

- Add multi-digit binary numbers using a full-adder for each bit.
- Problem: How to compute the carry-in for adder n ?

Copyright © 2002–2018 UMaine Computer Science Department – 22 / 29

Computing Carries: Ripple Carry

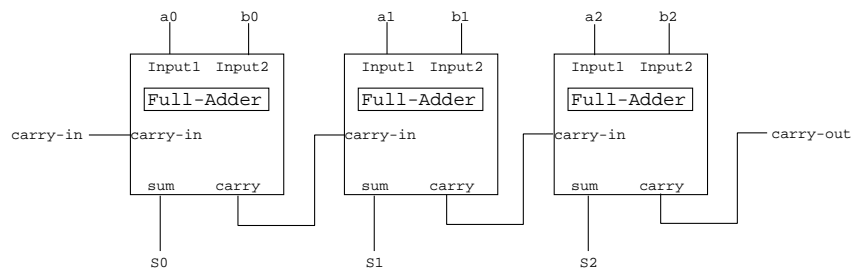- Hook up required number of full adders.
- As carry is calculated, passed to next bit.



Copyright © 2002–2018 UMaine Computer Science Department – 23 / 29

Computing Carries: Carry Lookahead

- First calculate what carry bits would be, based on previous bits
- Another way to specify carry-out is: carry-out of any full-adder (C_n) is true if:
 - carry-out of the first half-adder ($A_n B_n$) is true, or
 - either one of the inputs and the carry-in is true: $(A_n + B_n)C_{n-1}$
- So: $C_n = A_n B_n + (A_n + B_n)C_{n-1}$ – a *recurrence relation*

Copyright © 2002–2018 UMaine Computer Science Department – 24 / 29

Computing Carries: Carry Lookahead

- We can calculate any carry using the recurrence relation:

$$C_n = A_n B_n + (A_n + B_n)C_{n-1}$$

- $C_0 = A_0 B_0$, assuming no carry-in to low-order bit
- $C_1 = A_1 B_1 + (A_1 + B_1)C_0 \Rightarrow$
 $C_1 = A_1 B_1 + (A_1 + B_1)A_0 B_0$
- $C_2 = A_2 B_2 + (A_2 + B_2)C_1 \Rightarrow$
 $C_2 = A_2 B_2 + (A_2 + B_2)(A_1 B_1 + (A_1 + B_1)A_0 B_0)$
- ...

Copyright © 2002–2018 UMaine Computer Science Department – 25 / 29

Computing Carries: Carry Lookahead

- Alternative could be done using \oplus :
 - For carry-out of the first full-adder (C_0), it's the carry-out of the full-adder's first half-adder OR'd with the carry-out of the second:
 $C_0 = C_{0h} \vee C_{0f} \Rightarrow$
 $C_0 = A_0B_0 \vee S_0C_{in} \Rightarrow$
 $C_0 = A_0B_0 \vee (A_0 \oplus B_0)C_{in}$
 - C_1 is computable based on C_0 in the same way: $C_1 = A_1B_1 \vee (A_1 \oplus B_1)C_0 \Rightarrow$
 $C_1 = A_1B_1 \vee (A_1 \oplus B_1)(A_0B_0 \vee (A_0 \oplus B_0)C_{in})$
 - Can generalize to n bits
- But better to keep with ANDs and ORs

Copyright © 2002–2018 UMaine Computer Science Department – 26 / 29


Trade-offs for Types of Carry Propagation

- Ripple carry has larger delay.
 - Ripple carry has delay as more significant binary digits wait for results from less significant digits.
 - Carry lookahead uses a sum of products to get result for each carry, so only a two gate delay (have an AND layer and an OR layer).
- Complexity of circuit.
 - Ripple carry requires only connecting carry-out to next carry-in.
 - Number of AND gates and number of inputs to OR gate is **on the order** of the number of digits for carry lookahead (i.e., $O(n)$, where n is the number of digits)

Copyright © 2002–2018 UMaine Computer Science Department – 27 / 29

Combining Ripple Carry and Carry Lookahead

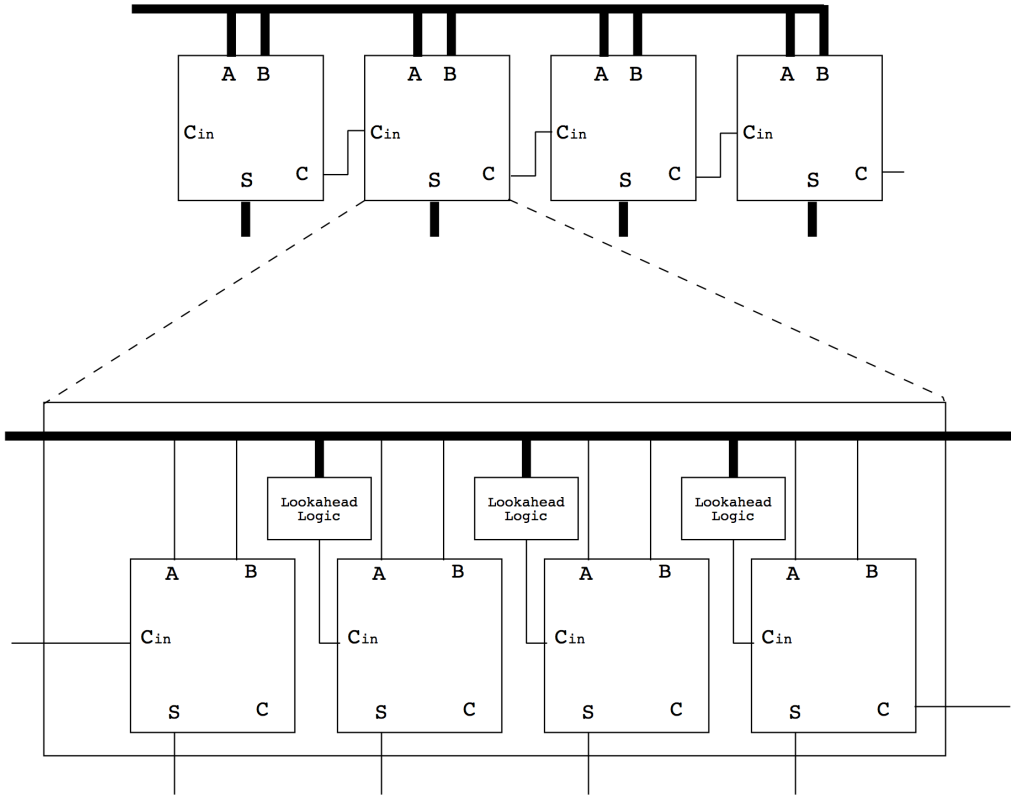- Minimize complexity of carry lookahead by only using it on a small number of bits in a group.
- Put groups together with a ripple carry.



Copyright © 2002–2018 UMaine Computer Science Department – 28 / 29

What have we learned?

- Combinational circuits are important for computers
- Sometimes direct minimization of circuits via SOP may not be best...
- ... need to think outside the mechanistic box!
- Easy way of combining circuits may not be best way
 - Sometimes best way requires a lot of work to find
 - Sometimes “best” may not have a single meaning...
 - ... may have to trade off (e.g.) time for circuit complexity
- Sometimes what looks hard to implement (carry lookahead) may not be (2 layers of gates)

Copyright © 2002–2018 UMaine Computer Science Department – 29 / 29