

Homework

- Reading: Chapter 9
- Homework: Chapter 9, exercises 1–4 & 7
- Due Monday, October 1

COS 140: Foundations of Computer Science

Parallel Registers

Fall 2018

Overview	3
Problem	3
Solution	4
Example	5
Circuits that Remember	6
Sequential Circuits	7
SR Latch	8
Characteristic Table	9
SR Latch Behavior	10
How It Works	11
Resetting	12
Input is 1 ?	13
Timing Diagrams	14
Clocked Latches	16
Registers	17
Requirements	17
Construction	18
One Bit	19
Two bits	20
Using the Register	21
More...	22
Flip-flops	23
Edge-triggering	24
SR flip-flop	25
MS flip-flops	26

Problem


- The *central processing unit* (CPU) needs some *memory*
 - Place to store instructions being executed
 - Place to store instruction's *operands*
 - Place to store intermediate values, output of calculations
- This memory has to be extremely fast: faster than RAM

Solution: Parallel Registers

- Use *parallel registers*
- Very fast type of memory
- Stores several bits at a time, function together as a unit.
- Could be one chip or more than one chip used in parallel
- Most often: part of the CPU

Copyright © 2002–2018 UMaine Computer Science Department – 4 / 26

A Parallel Register

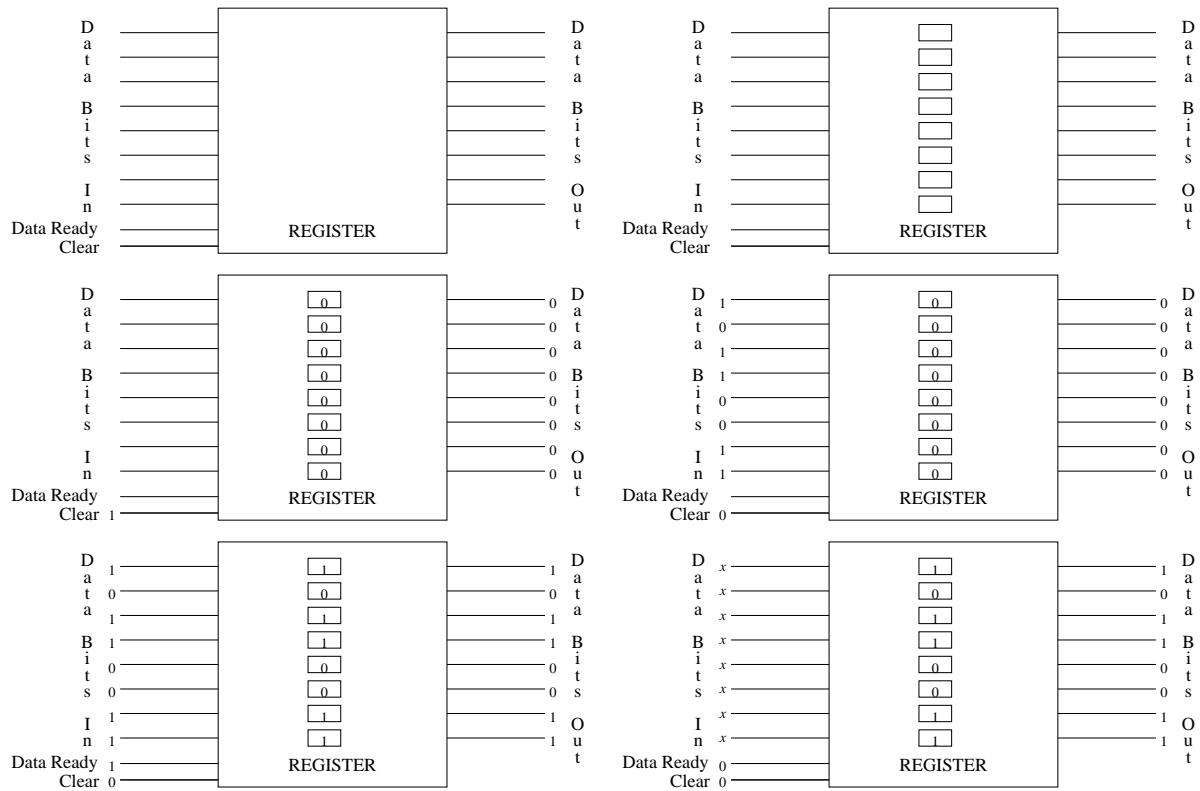

Copyright © 2002–2018 UMaine Computer Science Department – 5 / 26

WANTED: A Circuit that Can Remember

- To be useful for memory, the circuit must:
 - Be readable.
 - Maintain the current data, unless its inputs tell it to change.
 - Allow the data to be changed.
- Combination circuits have outputs that are a function only of inputs, so no ability to maintain the current data.


Copyright © 2002–2018 UMaine Computer Science Department – 6 / 26

Sequential Circuits

- Have **state** which can be 0 or 1.
- New state depends on inputs and previous state.
- Often have *clock* (strobe, enable) that allows input to enter the circuit only at particular times.
- Sequential circuits work for memory because
 - The current state can be easily read from its output (packaging often makes the state's complement available as well)
 - Some set of inputs (usually all 0's) cause it to maintain state
 - Other inputs can change the data

Copyright © 2002–2018 UMaine Computer Science Department – 7 / 26

 A Circuit that Can Maintain State: The S-R Latch



- Can be set (with S) and reset (with R)
- Maintains whatever state it's set to when inputs removed (set to 0)

Copyright © 2002–2018 UMaine Computer Science Department – 8 / 26

Characteristic Table

- How to specify the behavior of a sequential circuit?
- Truth table won't work: doesn't reference current state
- Instead, use a *characteristic table*; like a truth table, but:
 - Shows current state as well as inputs
 - Gives new state (which is output as well)
 - Note: Can have inputs for which there is no stable state, an undefined state, or a state that does not make sense

Copyright © 2002–2018 UMaine Computer Science Department – 9 / 26


What Would We Expect?

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	-

Copyright © 2002–2018 UMaine Computer Science Department – 10 / 26


How the S-R Latch Maintains State

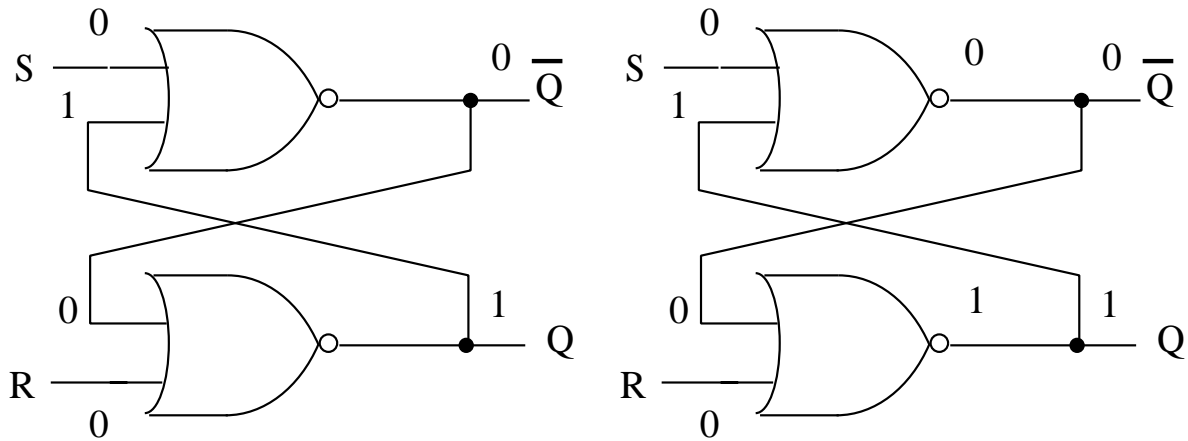Have feedback from the current state and its complement that act as input to the circuit.




Copyright © 2002–2018 UMaine Computer Science Department – 11 / 26

How the S-R Latch's State Is Reset to 0

 

Copyright © 2002–2018 UMaine Computer Science Department – 12 / 26


What Happens with 1 1 Input?

 

- State not reasonable: $Q = \overline{Q}$.
- What happens when $S = R = 0$?
- If absolutely no difference in timing, gate delays: oscillation (very unlikely)
- With different gate delay or, timing of S & R \Rightarrow random stable state


Copyright © 2002–2018 UMaine Computer Science Department – 13 / 26

Timing Diagrams

 

Copyright © 2002–2018 UMaine Computer Science Department – 14 / 26


Timing Diagrams

 

Copyright © 2002–2018 UMaine Computer Science Department – 15 / 26

Clocked Latches

 - Sometimes you want the state to change only at certain times.
- To do this, latches can be hooked to a clock.
- The clock is a signal that is 1 at certain intervals.
- Creating clocks in hardware and dealing with timing issues in circuits is a complex problem...beyond the scope of this course.



- If clock is not 1, equivalent to S and R of unlocked latch being 0, and maintain state. If clock is 1, value of S and R get through AND gate.

Copyright © 2002–2018 UMaine Computer Science Department – 16 / 26

Registers

17 / 26

What Do We Need in a Register?

- Each bit can be stored in a latch (usually 8 or more)
- Nice to be able to reset register to all 0's
- Output available from each bit
- Input can be directed to each bit


Copyright © 2002–2018 UMaine Computer Science Department – 17 / 26

How Can We Construct a Register?

- We can use S-R Latches and simply make sure S and R are not both 1 at the same time.
- Have a reset line that goes to R in each latch.
- “Strobe” input and output so that write or read data only at specific times. (Works similarly to a clock.)


Copyright © 2002–2018 UMaine Computer Science Department – 18 / 26

One Bit of a Register

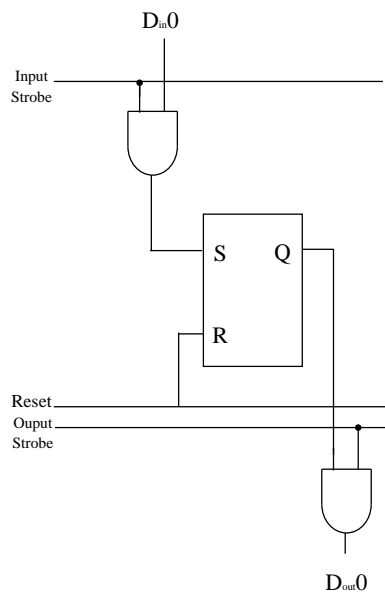


Copyright © 2002–2018 UMaine Computer Science Department – 19 / 26

A Two-Bit Piece of a Register

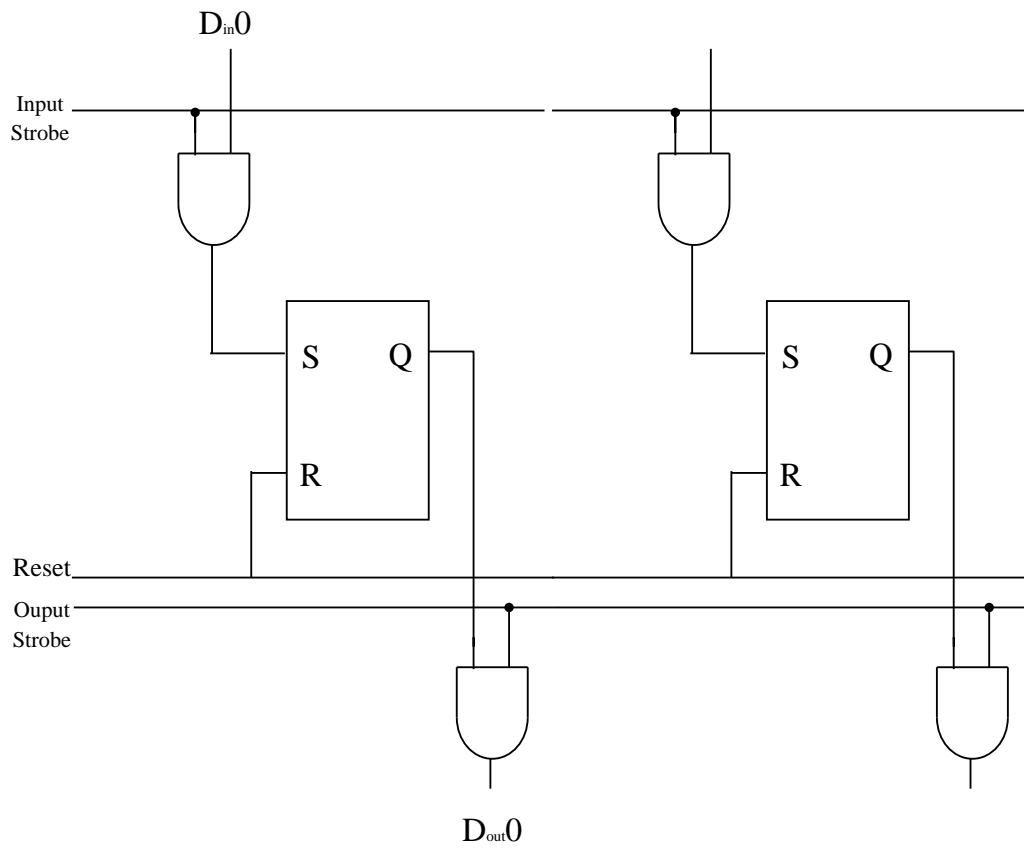

Using the Register

 

Can we just put in the data? What happens if the new data is 0, but the previous data was 1? What can we do to fix this?

Need to reset each time before loading data.


More About Latches and Registers

- There are other kinds of latches which:
 - Do not require resetting register before loading data – so can toggle individual bits
 - Handle the problem of 1–1 inputs
- Registers can be constructed out of these latches, as well.

Copyright © 2002–2018 UMaine Computer Science Department – 22 / 26

Flip-flops

 - So far: *latches – level-triggered*
- Problem:
 - Only want changes once per clock pulse
 - But: clock pulse can be long \Rightarrow time for inputs to change
 - Could lead to unwanted states: e.g., 1–1 to SR latch




- Solution: *edge-triggering*
- Edge-triggered latch \equiv *flip-flop*


Copyright © 2002–2018 UMaine Computer Science Department – 23 / 26

Edge-triggering

 - Problem: How to trigger only on *edge* of clock pulse?
- One way: use *pulse detector* circuit
- Can use gate delays to our advantage:




- Gives this behavior:

 

Copyright © 2002–2018 UMaine Computer Science Department – 24 / 26

SR flip-flop

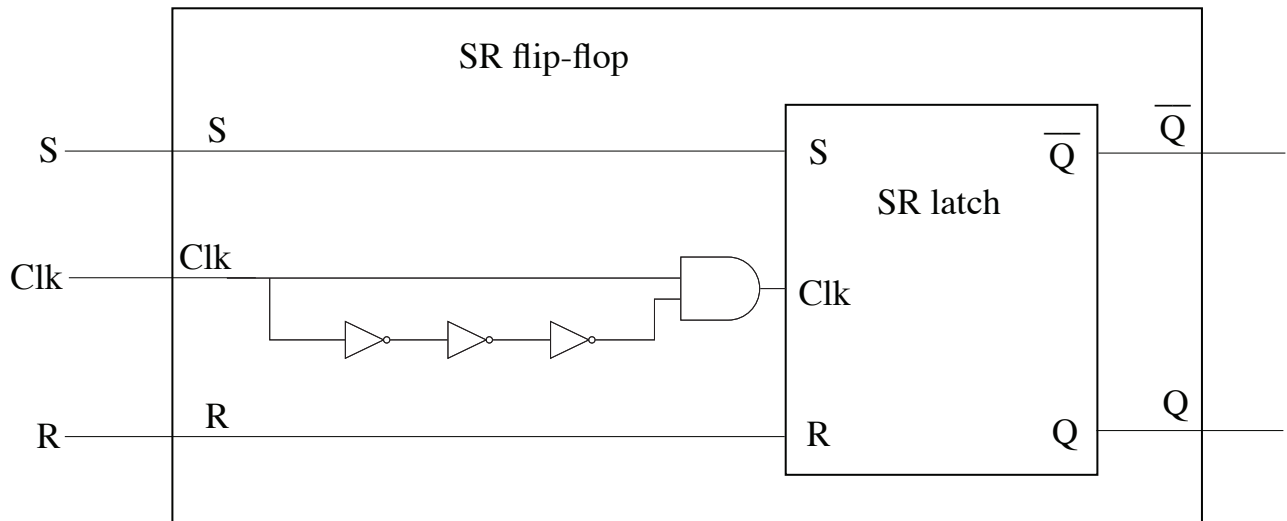- Put pulse detector on clock of clocked latch \Rightarrow flip-flop



Copyright © 2002–2018 UMaine Computer Science Department – 25 / 26

Edge triggering: master-slave configuration

- Can also get edge triggering by using two latches:

