

# Homework

Overview

Circuits that Remember

Registers

- Reading: Chapter 9
- Homework: Chapter 9, exercises 1–4 & 7
- Due Monday, October 1

# COS 140: Foundations of Computer Science

## Parallel Registers

Fall 2018

# Problem

Overview

● Problem

● Solution

● Example

Circuits that Remember

Registers

- The *central processing unit* (CPU) needs some *memory*
  - Place to store instructions being executed
  - Place to store instruction's *operands*
  - Place to store intermediate values, output of calculations
- This memory has to be extremely fast: faster than RAM

# Solution: Parallel Registers

## Overview

- Problem
- **Solution**
- Example

## Circuits that Remember

### Registers

- Use *parallel registers*
- Very fast type of memory
- Stores several bits at a time, function together as a unit.
- Could be one chip or more than one chip used in parallel
- Most often: part of the CPU


# A Parallel Register

## Overview

- Problem
- Solution
- Example

## Circuits that Remember

## Registers

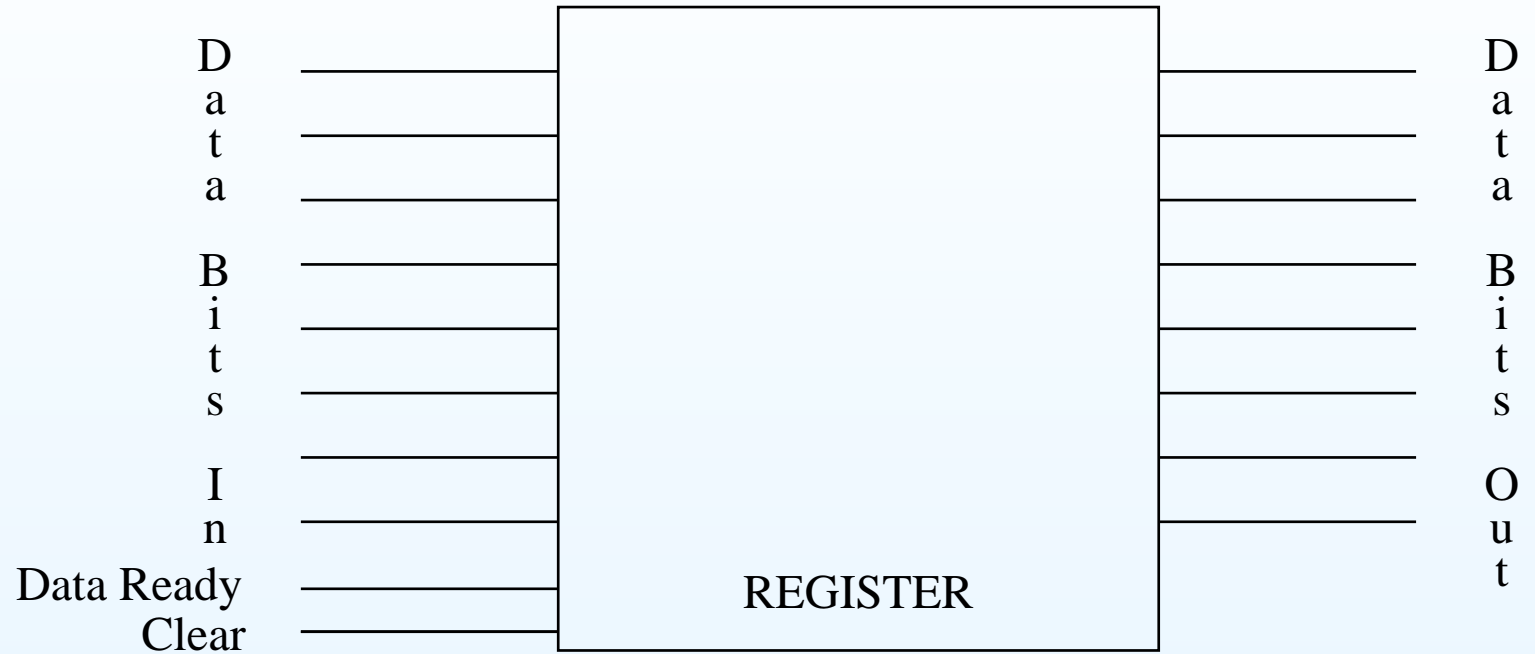


# A Parallel Register

## Overview

- Problem
- Solution
- Example

## Circuits that Remember

### Registers

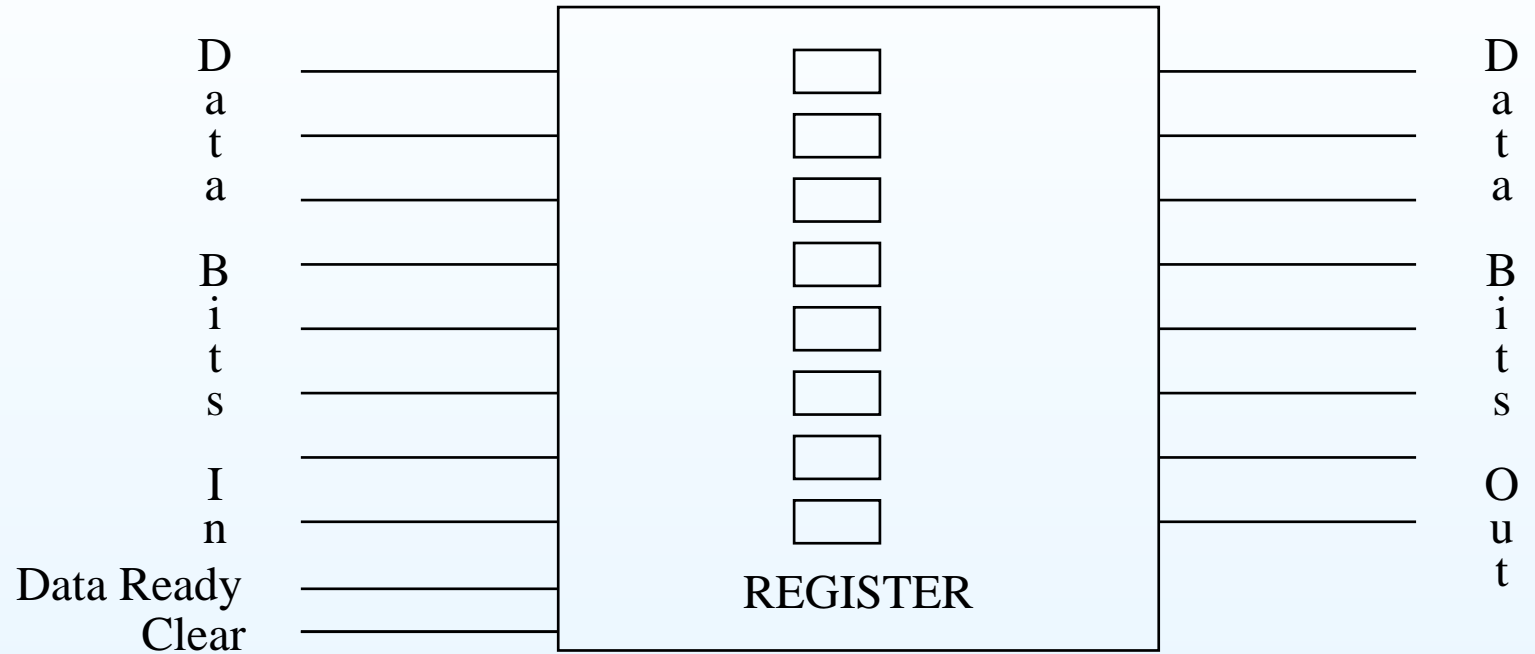


# A Parallel Register

## Overview

- Problem
- Solution
- Example

## Circuits that Remember

### Registers

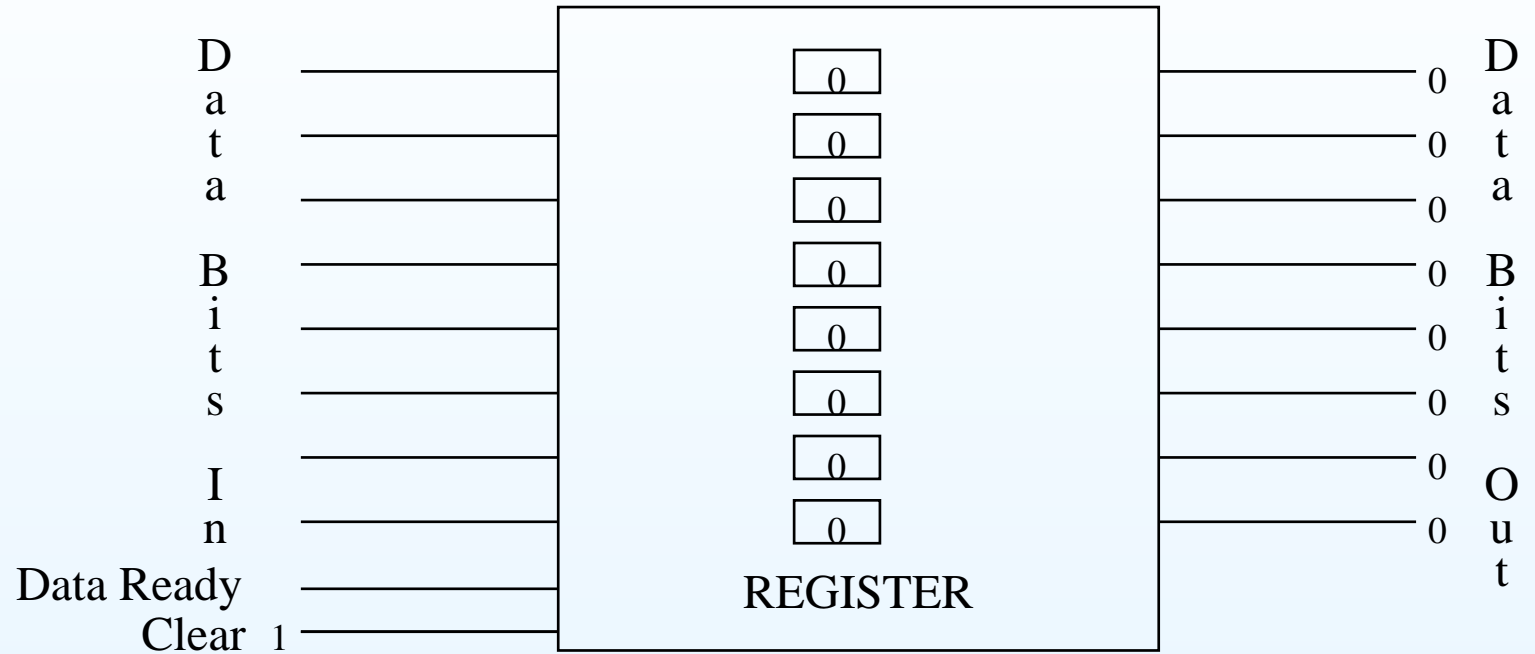


# A Parallel Register

## Overview

- Problem
- Solution
- Example

## Circuits that Remember

### Registers

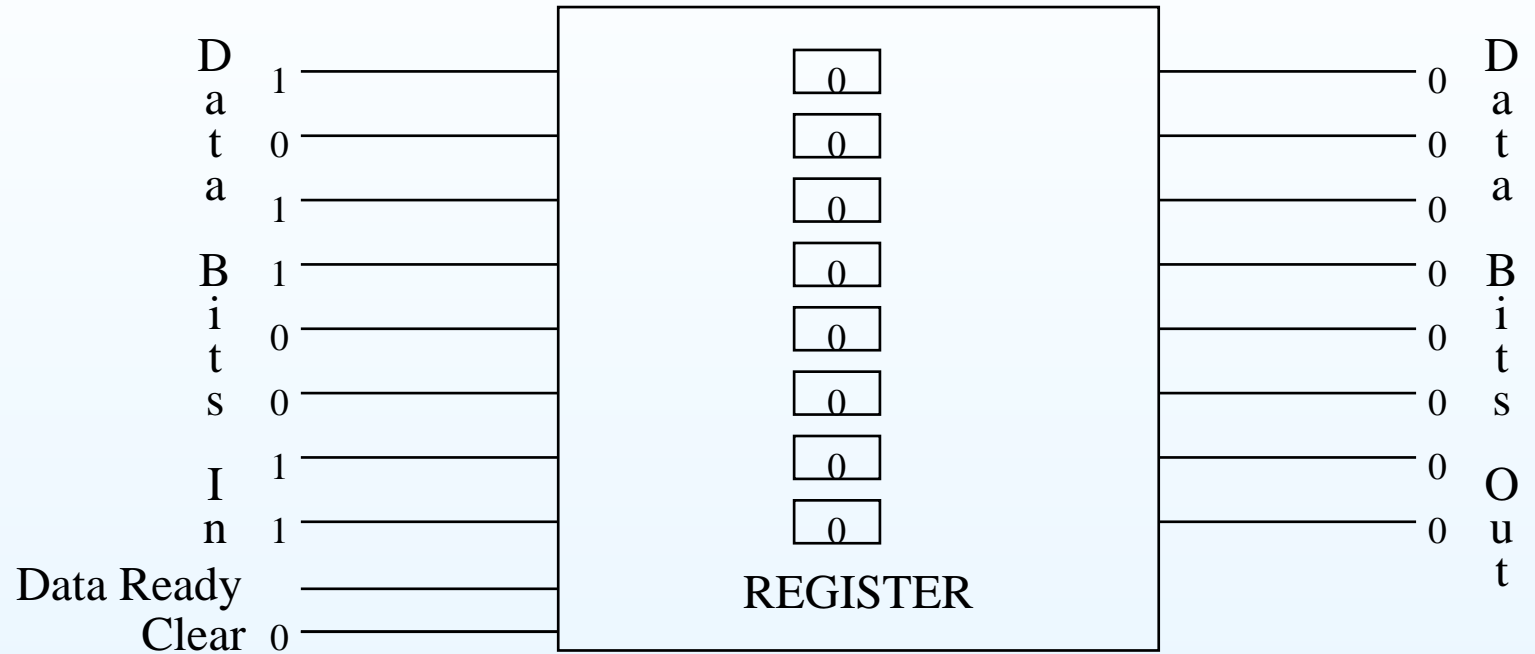




# A Parallel Register

## Overview

- Problem
- Solution
- Example

## Circuits that Remember

### Registers

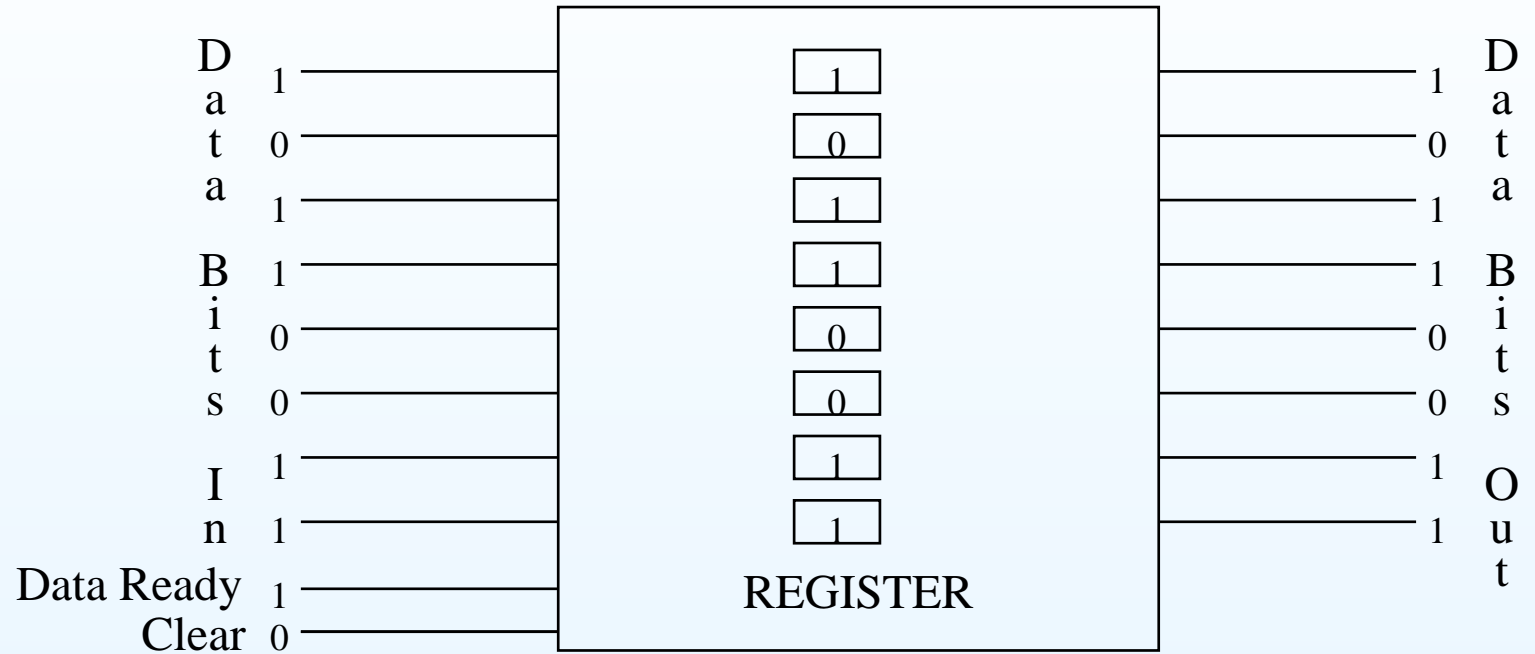


# A Parallel Register

## Overview

- Problem
- Solution
- Example

## Circuits that Remember

### Registers

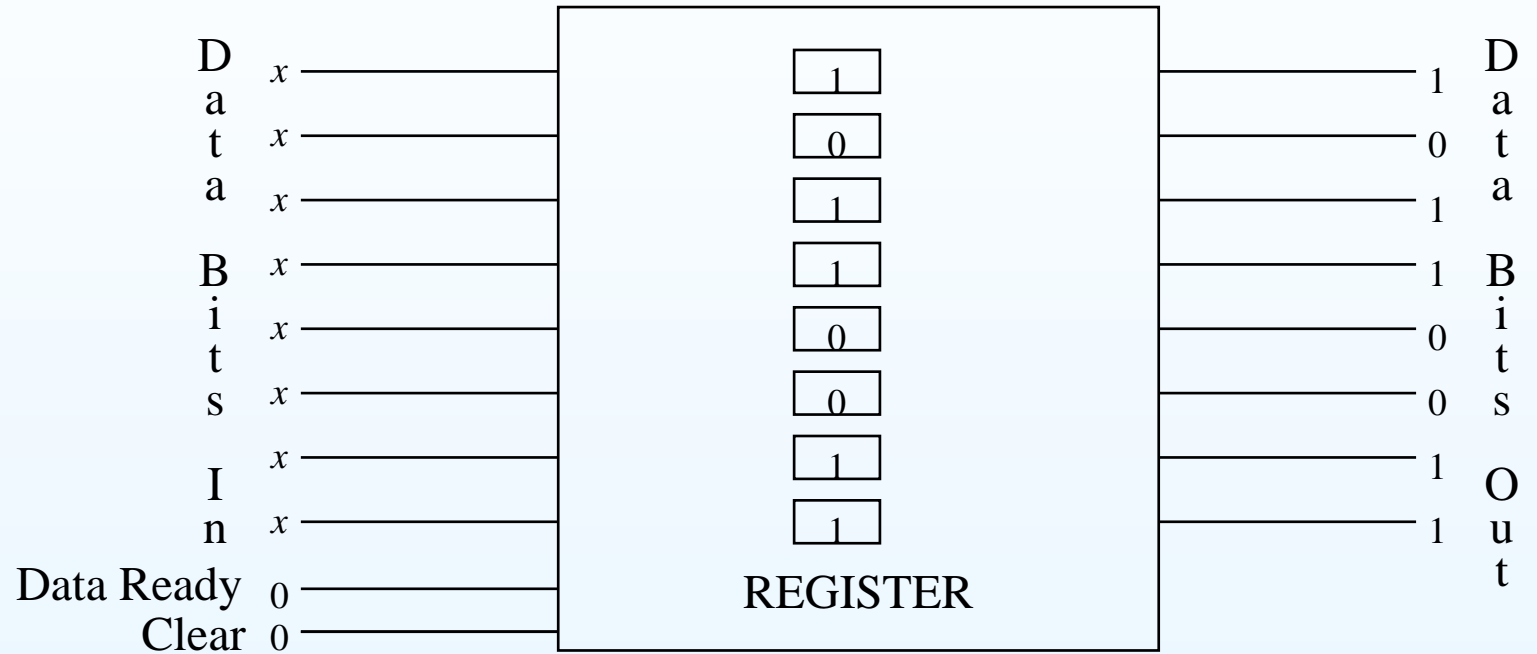

# WANTED: A Circuit that Can Remember

Overview

Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

Registers

- To be useful for memory, the circuit must:

# WANTED: A Circuit that Can Remember

Overview

**Circuits that Remember**

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

Registers

- To be useful for memory, the circuit must:
  - Be readable.

# WANTED: A Circuit that Can Remember

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

## Registers

- To be useful for memory, the circuit must:
  - Be readable.
  - Maintain the current data, unless its inputs tell it to change.

# WANTED: A Circuit that Can Remember

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

## Registers

- To be useful for memory, the circuit must:
  - Be readable.
  - Maintain the current data, unless its inputs tell it to change.
  - Allow the data to be changed.

# WANTED: A Circuit that Can Remember

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

## Registers

- To be useful for memory, the circuit must:
  - Be readable.
  - Maintain the current data, unless its inputs tell it to change.
  - Allow the data to be changed.
- Combination circuits have outputs that are a function only of inputs, so no ability to maintain the current data.

# Sequential Circuits

## Overview

### Circuits that Remember

- **Sequential Circuits**

- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

### Registers

- Have **state** which can be 0 or 1.
- New state depends on inputs and previous state.
- Often have **clock** (strobe, enable) that allows input to enter the circuit only at particular times.
- Sequential circuits work for memory because
  - The current state can be easily read from its output (packaging often makes the state's complement available as well)
  - Some set of inputs (usually all 0's) cause it to maintain state
  - Other inputs can change the data




# A Circuit that Can Maintain State: The S-R Latch

## Overview

### Circuits that Remember

- Sequential Circuits
- **SR Latch**
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

### Registers

 

- Can be set (with S) and reset (with R)
- Maintains whatever state it's set to when inputs removed (set to 0)

# Characteristic Table

## Overview

## Circuits that Remember

- Sequential Circuits
- SR Latch
- **Characteristic Table**
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

## Registers

- How to specify the behavior of a sequential circuit?

# Characteristic Table

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- **Characteristic Table**
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

## Registers

- How to specify the behavior of a sequential circuit?
- Truth table won't work: doesn't reference current state
- Instead, use a *characteristic table*; like a truth table, but:
  - Shows current state as well as inputs
  - Gives new state (which is output as well)
  - Note: Can have inputs for which there is no stable state, an undefined state, or a state that does not make sense

# What Would We Expect?

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- **SR Latch Behavior**
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

### Registers

# What Would We Expect?

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- **SR Latch Behavior**
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

### Registers

S	R	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	-

## How the S-R Latch Maintains State


### Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- **How It Works**
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches
 
### Registers

Have feedback from the current state and its complement that act as input to the circuit.



Suppose initial state is 1 and complement is 0. S and R are both 0 (neither set or reset).

## How the S-R Latch Maintains State


### Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- **How It Works**
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches
 
### Registers

Have feedback from the current state and its complement that act as input to the circuit.



Suppose initial state is 1 and complement is 0. S and R are both 0 (neither set or reset).


## How the S-R Latch's State Is Reset to 0

### Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- **Resetting**
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

### Registers

 




# How the S-R Latch's State Is Reset to 0

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- **Resetting**
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

### Registers

 


# How the S-R Latch's State Is Reset to 0

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- **Resetting**
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

### Registers

 


# How the S-R Latch's State Is Reset to 0

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- **Resetting**
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

### Registers

 


# How the S-R Latch's State Is Reset to 0

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- **Resetting**
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

### Registers

 


# How the S-R Latch's State Is Reset to 0

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- **Resetting**
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

### Registers

 


# What Happens with 1 1 Input?

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- **Input is 1 1?**
- Timing Diagrams
- Clocked Latches

### Registers

 


# What Happens with 1 1 Input?

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- **Input is 1 1?**
- Timing Diagrams
- Clocked Latches

### Registers

 


# What Happens with 1 1 Input?

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- **Input is 1 1?**
- Timing Diagrams
- Clocked Latches

## Registers

 

- State not reasonable:  $Q = \overline{Q}$ .




# What Happens with 1 1 Input?

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- **Input is 1 1?**
- Timing Diagrams
- Clocked Latches

### Registers

 

- State not reasonable:  $Q = \overline{Q}$ .
- What happens when  $S = R = 0$ ?


# What Happens with 1 1 Input?

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- **Input is 1 1?**
- Timing Diagrams
- Clocked Latches

### Registers

 

- State not reasonable:  $Q = \overline{Q}$ .
- What happens when  $S = R = 0$ ?


# What Happens with 1 1 Input?

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- **Input is 1 1?**
- Timing Diagrams
- Clocked Latches

### Registers

 

- State not reasonable:  $Q = \overline{Q}$ .
- What happens when  $S = R = 0$ ?


# What Happens with 1 1 Input?

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- **Input is 1 1?**
- Timing Diagrams
- Clocked Latches

## Registers

 

- State not reasonable:  $Q = \overline{Q}$ .
- What happens when  $S = R = 0$ ?


# What Happens with 1 1 Input?

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- **Input is 1 1?**
- Timing Diagrams
- Clocked Latches

### Registers

 

- State not reasonable:  $Q = \overline{Q}$ .
- What happens when  $S = R = 0$ ?


# What Happens with 1 1 Input?

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- **Input is 1 1?**
- Timing Diagrams
- Clocked Latches

## Registers

 

- State not reasonable:  $Q = \bar{Q}$ .
- What happens when  $S = R = 0$ ?
- If absolutely no difference in timing, gate delays: oscillation (very unlikely)


# What Happens with 1 1 Input?

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- **Input is 1 1?**
- Timing Diagrams
- Clocked Latches

### Registers

 

- State not reasonable:  $Q = \overline{Q}$ .
- What happens when  $S = R = 0$ ?
- If absolutely no difference in timing, gate delays: oscillation (very unlikely)
- With different gate delay or, timing of S & R  $\Rightarrow$  random stable state


# Timing Diagrams

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- **Timing Diagrams**
- Clocked Latches

### Registers

 





# Timing Diagrams

## Overview

## Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- **Timing Diagrams**
- Clocked Latches

## Registers

  


# Timing Diagrams

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- **Timing Diagrams**
- Clocked Latches

### Registers

 



# Clocked Latches

## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches

### Registers

- Sometimes you want the state to change only at certain times.
- To do this, latches can be hooked to a clock.
- The clock is a signal that is 1 at certain intervals.
- Creating clocks in hardware and dealing with timing issues in circuits is a complex problem...beyond the scope of this course.

# Clocked Latches


## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches
 
## Registers

- Sometimes you want the state to change only at certain times.
- To do this, latches can be hooked to a clock.
- The clock is a signal that is 1 at certain intervals.
- Creating clocks in hardware and dealing with timing issues in circuits is a complex problem...beyond the scope of this course.



# Clocked Latches


## Overview

### Circuits that Remember

- Sequential Circuits
- SR Latch
- Characteristic Table
- SR Latch Behavior
- How It Works
- Resetting
- Input is 1 1?
- Timing Diagrams
- Clocked Latches
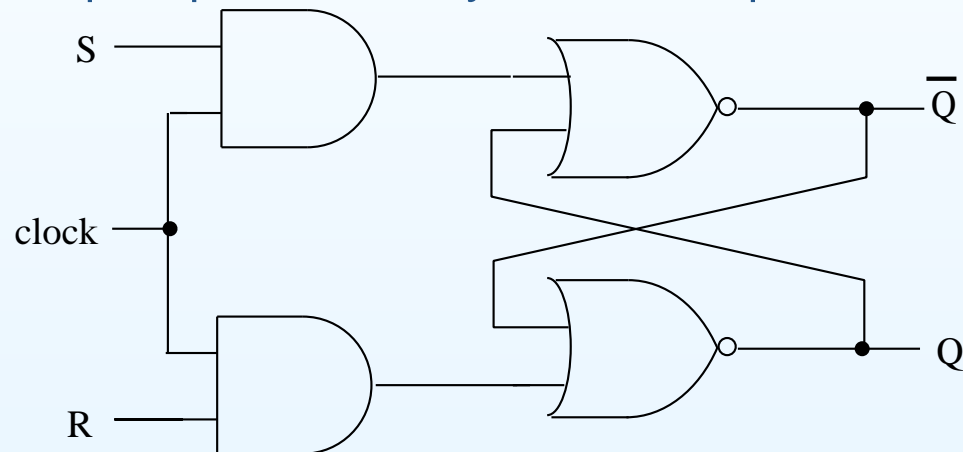
### Registers

- Sometimes you want the state to change only at certain times.
- To do this, latches can be hooked to a clock.
- The clock is a signal that is 1 at certain intervals.
- Creating clocks in hardware and dealing with timing issues in circuits is a complex problem...beyond the scope of this course.



- If clock is not 1, equivalent to S and R of unlocked latch being 0, and maintain state. If clock is 1, value of S and R get through AND gate.

# What Do We Need in a Register?

Overview

Circuits that Remember

Registers

- **Requirements**

- Construction
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- Edge-triggering
- SR flip-flop
- MS flip-flops

- Each bit can be stored in a latch (usually 8 or more)
- Nice to be able to reset register to all 0's
- Output available from each bit
- Input can be directed to each bit

# How Can We Construct a Register?

Overview

Circuits that Remember

Registers

- Requirements
- **Construction**
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- Edge-triggering
- SR flip-flop
- MS flip-flops

- We can use S-R Latches and simply make sure S and R are not both 1 at the same time.
- Have a reset line that goes to R in each latch.
- “Strobe” input and output so that write or read data only at specific times. (Works similarly to a clock.)




# One Bit of a Register

Overview

Circuits that Remember

Registers

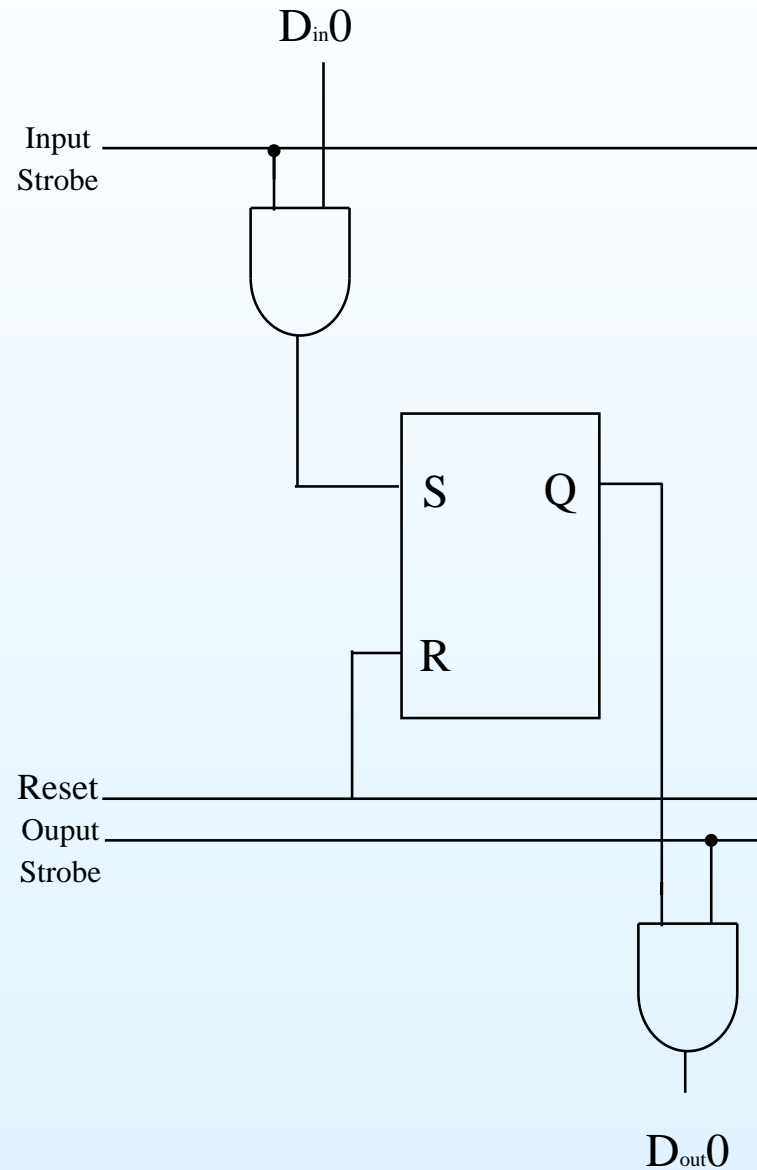- Requirements
- Construction
- **One Bit**
- Two bits
- Using the Register
- More...
- Flip-flops
- Edge-triggering
- SR flip-flop
- MS flip-flops




# A Two-Bit Piece of a Register

## Overview

## Circuits that Remember
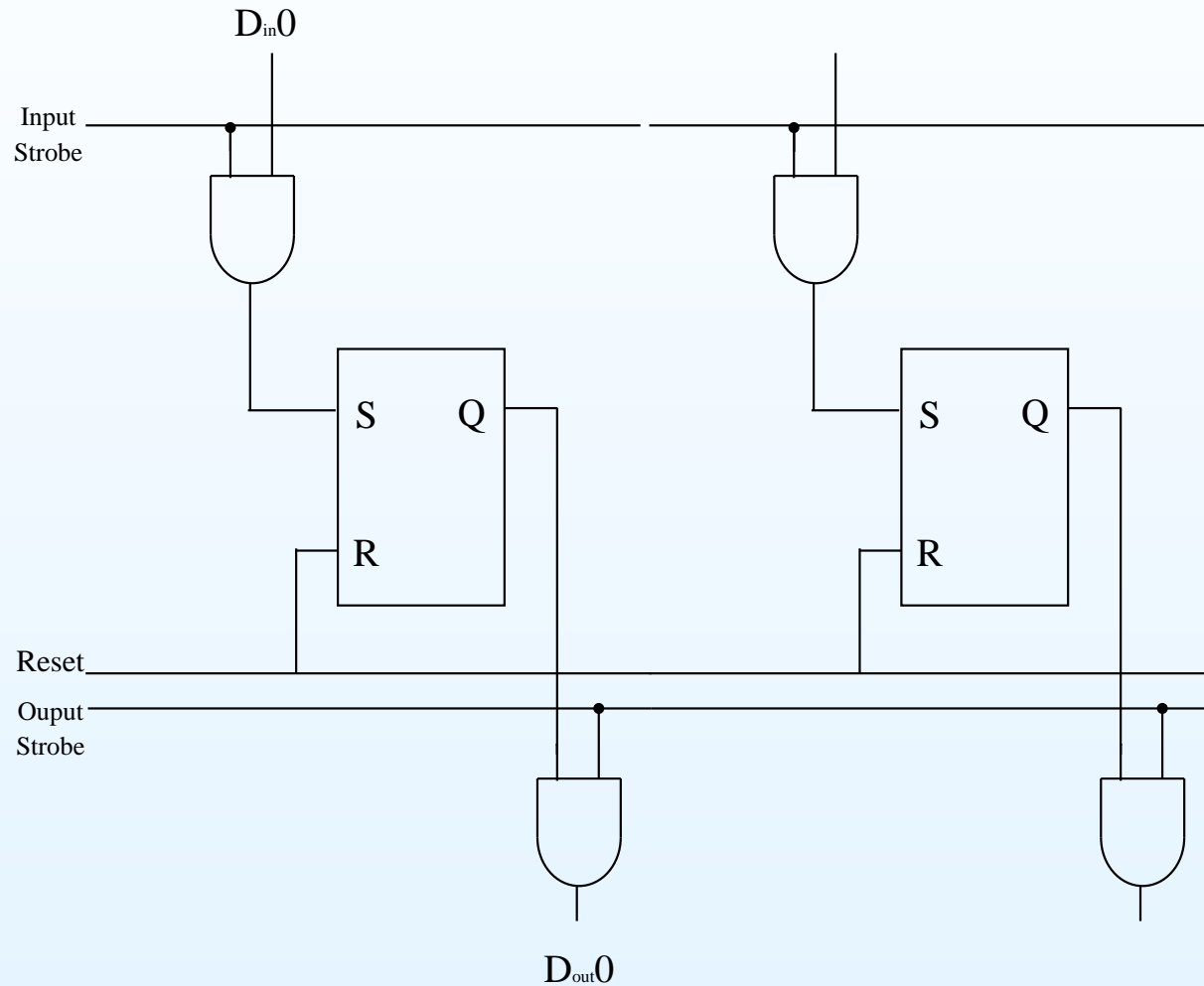
## Registers

- Requirements
- Construction
- One Bit
- **Two bits**
- Using the Register
- More...
- Flip-flops
- Edge-triggering
- SR flip-flop
- MS flip-flops




# Using the Register

## Overview

## Circuits that Remember
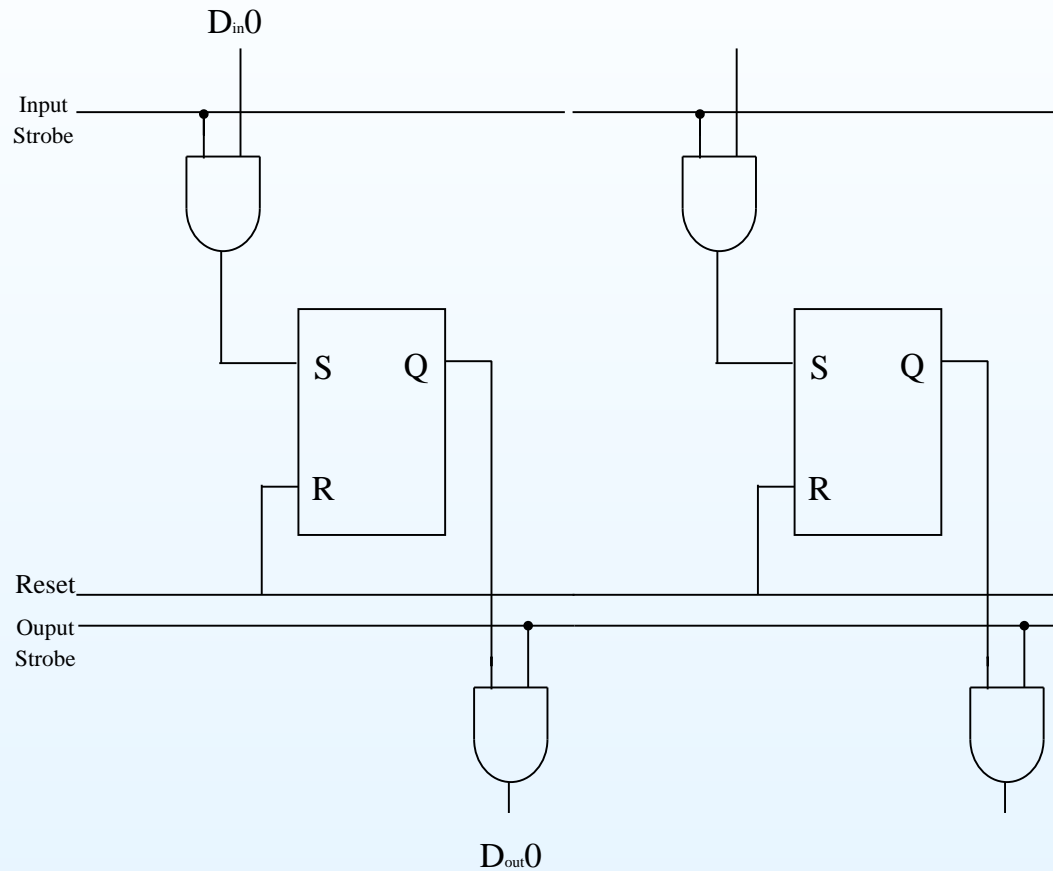
## Registers

- Requirements
- Construction
- One Bit
- Two bits
- **Using the Register**
- More...
- Flip-flops
- Edge-triggering
- SR flip-flop
- MS flip-flops



Can we just put in the data? What happens if the new data is 0, but the previous data was 1?


# Using the Register

## Overview

## Circuits that Remember
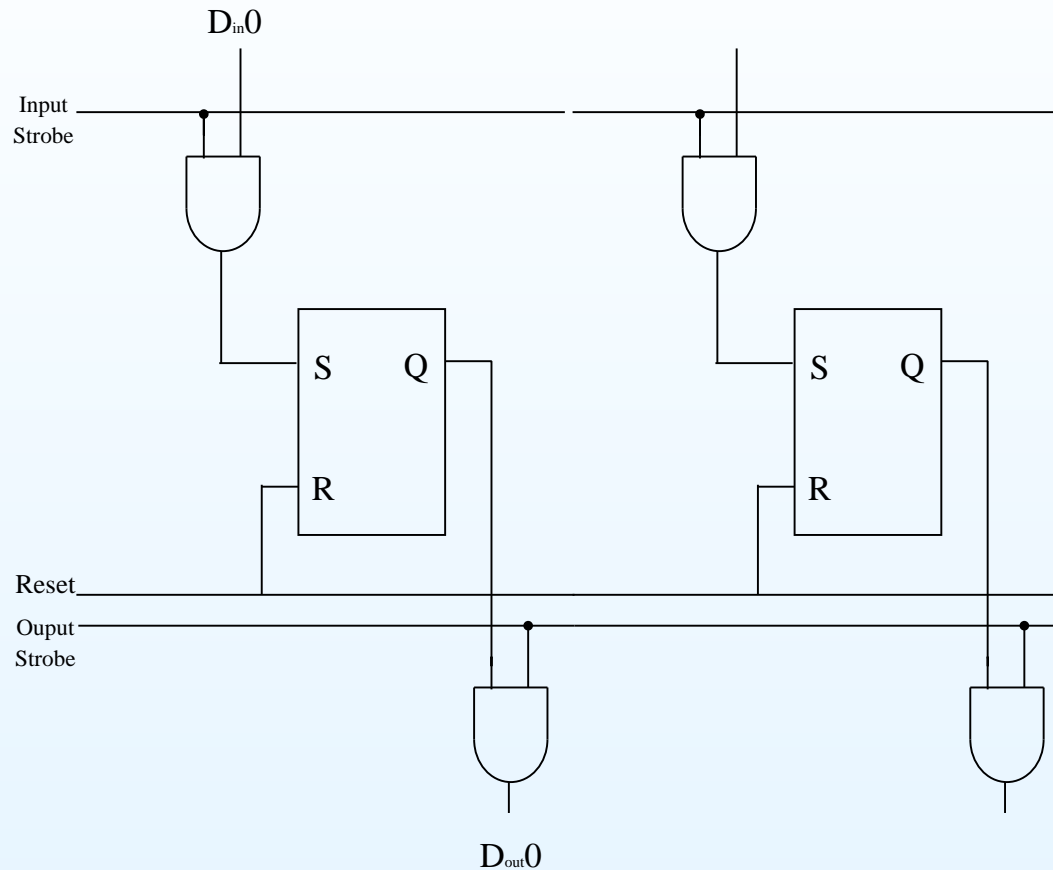
## Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- Edge-triggering
- SR flip-flop
- MS flip-flops



Can we just put in the data? What happens if the new data is 0, but the previous data was 1? What can we do to fix this?


# Using the Register

## Overview

## Circuits that Remember
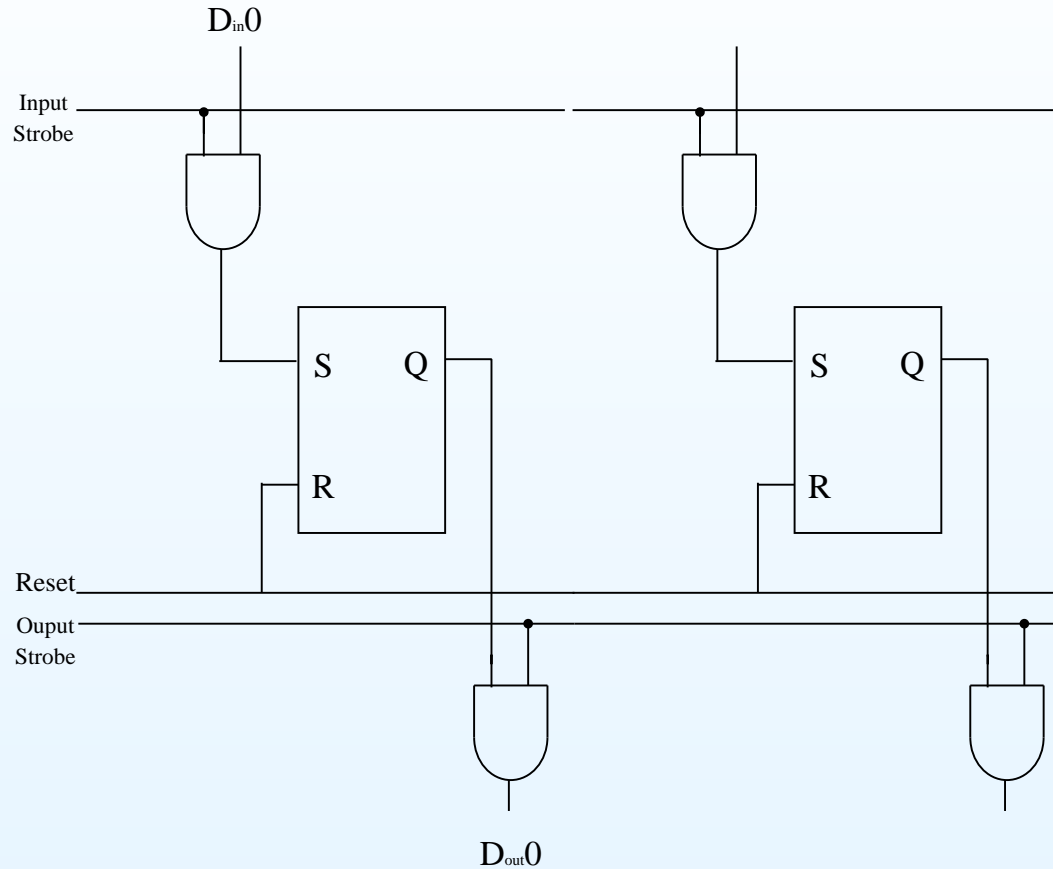
## Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- Edge-triggering
- SR flip-flop
- MS flip-flops



Can we just put in the data? What happens if the new data is 0, but the previous data was 1? What can we do to fix this?

Need to reset each time before loading data.

# More About Latches and Registers

Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- **More...**
- Flip-flops
- Edge-triggering
- SR flip-flop
- MS flip-flops

- There are other kinds of latches which:
  - Do not require resetting register before loading data – so can toggle individual bits
  - Handle the problem of 1–1 inputs
- Registers can be constructed out of these latches, as well.

# Flip-flops

Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- **Flip-flops**
- Edge-triggering
- SR flip-flop
- MS flip-flops

- So far: *latches* – *level-triggered*
- Problem:
  - Only want changes once per clock pulse
  - But: clock pulse can be long  $\Rightarrow$  time for inputs to change
  - Could lead to unwanted states: e.g., 1–1 to SR latch

# Flip-flops


Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- **Flip-flops**
- Edge-triggering
- SR flip-flop
- MS flip-flops

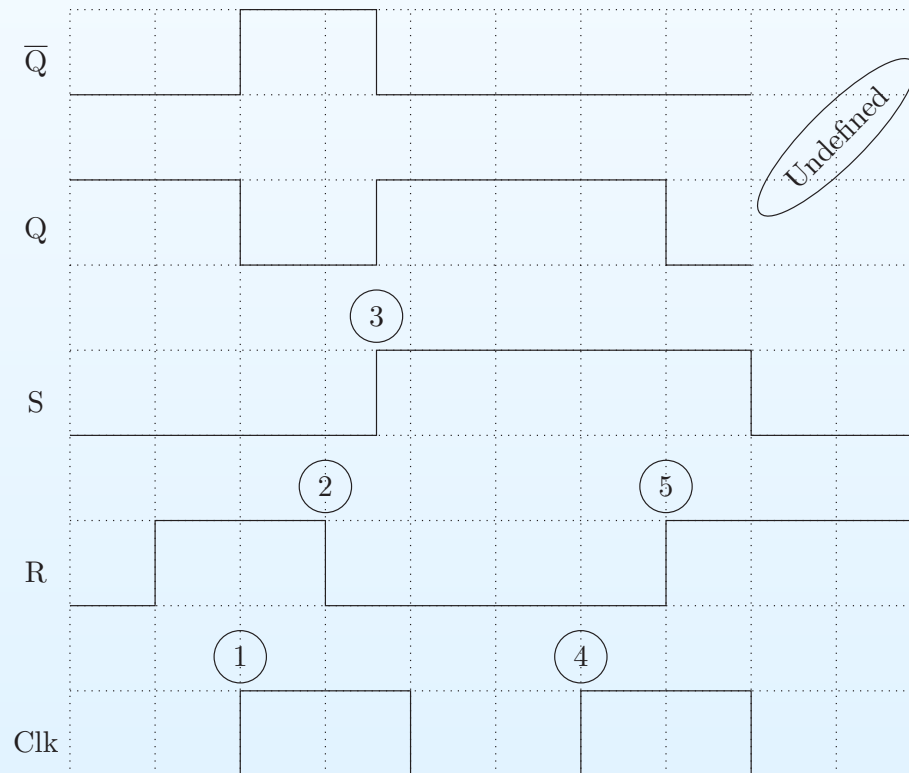- So far: *latches* – *level-triggered*
- Problem:
  - Only want changes once per clock pulse
  - But: clock pulse can be long  $\Rightarrow$  time for inputs to change
  - Could lead to unwanted states: e.g., 1–1 to SR latch





# Flip-flops

Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- **Flip-flops**
- Edge-triggering
- SR flip-flop
- MS flip-flops

- So far: *latches* – *level-triggered*
- Problem:
  - Only want changes once per clock pulse
  - But: clock pulse can be long  $\Rightarrow$  time for inputs to change
  - Could lead to unwanted states: e.g., 1–1 to SR latch
- Solution: *edge-triggering*

# Flip-flops

Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- **Flip-flops**
- Edge-triggering
- SR flip-flop
- MS flip-flops

- So far: *latches* – *level-triggered*
- Problem:
  - Only want changes once per clock pulse
  - But: clock pulse can be long  $\Rightarrow$  time for inputs to change
  - Could lead to unwanted states: e.g., 1–1 to SR latch
- Solution: *edge-triggering*
- Edge-triggered latch  $\equiv$  *flip-flop*

# Edge-triggering

Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- **Edge-triggering**
- SR flip-flop
- MS flip-flops

- Problem: How to trigger only on *edge* of clock pulse?

# Edge-triggering

Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- **Edge-triggering**
- SR flip-flop
- MS flip-flops

- Problem: How to trigger only on *edge* of clock pulse?
- One way: use *pulse detector* circuit

# Edge-triggering

Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- **Edge-triggering**
- SR flip-flop
- MS flip-flops

- Problem: How to trigger only on *edge* of clock pulse?
- One way: use *pulse detector* circuit
- Can use gate delays to our advantage:

# Edge-triggering


Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- **Edge-triggering**
- SR flip-flop
- MS flip-flops

 - Problem: How to trigger only on *edge* of clock pulse?
- One way: use *pulse detector* circuit
- Can use gate delays to our advantage:



# Edge-triggering


Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- **Edge-triggering**
- SR flip-flop
- MS flip-flops

 - Problem: How to trigger only on *edge* of clock pulse?
- One way: use *pulse detector* circuit
- Can use gate delays to our advantage:



- Gives this behavior:



# SR flip-flop

Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- Edge-triggering
- **SR flip-flop**
- MS flip-flops

- Put pulse detector on clock of clocked latch  $\Rightarrow$  flip-flop



# SR flip-flop


Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- Edge-triggering
- **SR flip-flop**
- MS flip-flops

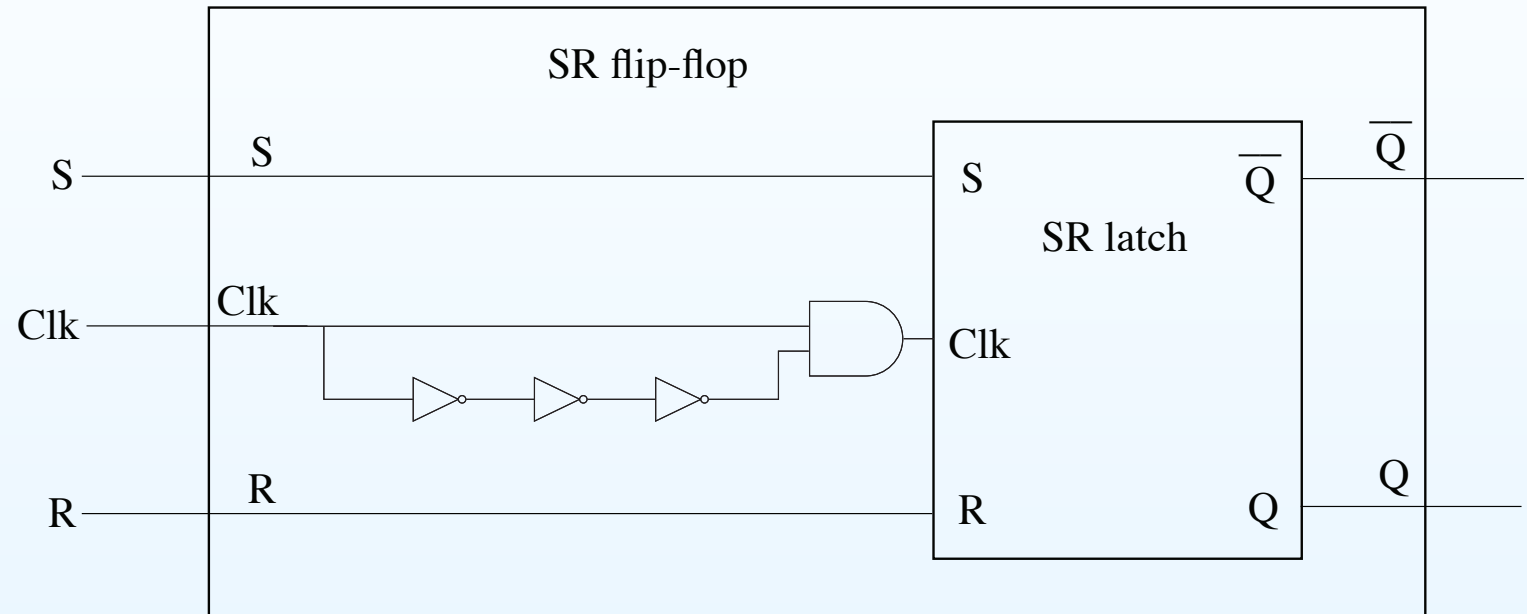- Put pulse detector on clock of clocked latch  $\Rightarrow$  flip-flop



# Edge triggering: master–slave configuration

Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- Edge-triggering
- SR flip-flop
- MS flip-flops

- Can also get edge triggering by using two latches:

# Edge triggering: master-slave configuration

Overview

Circuits that Remember

Registers

- Requirements
- Construction
- One Bit
- Two bits
- Using the Register
- More...
- Flip-flops
- Edge-triggering
- SR flip-flop
- MS flip-flops

- Can also get edge triggering by using two latches:

